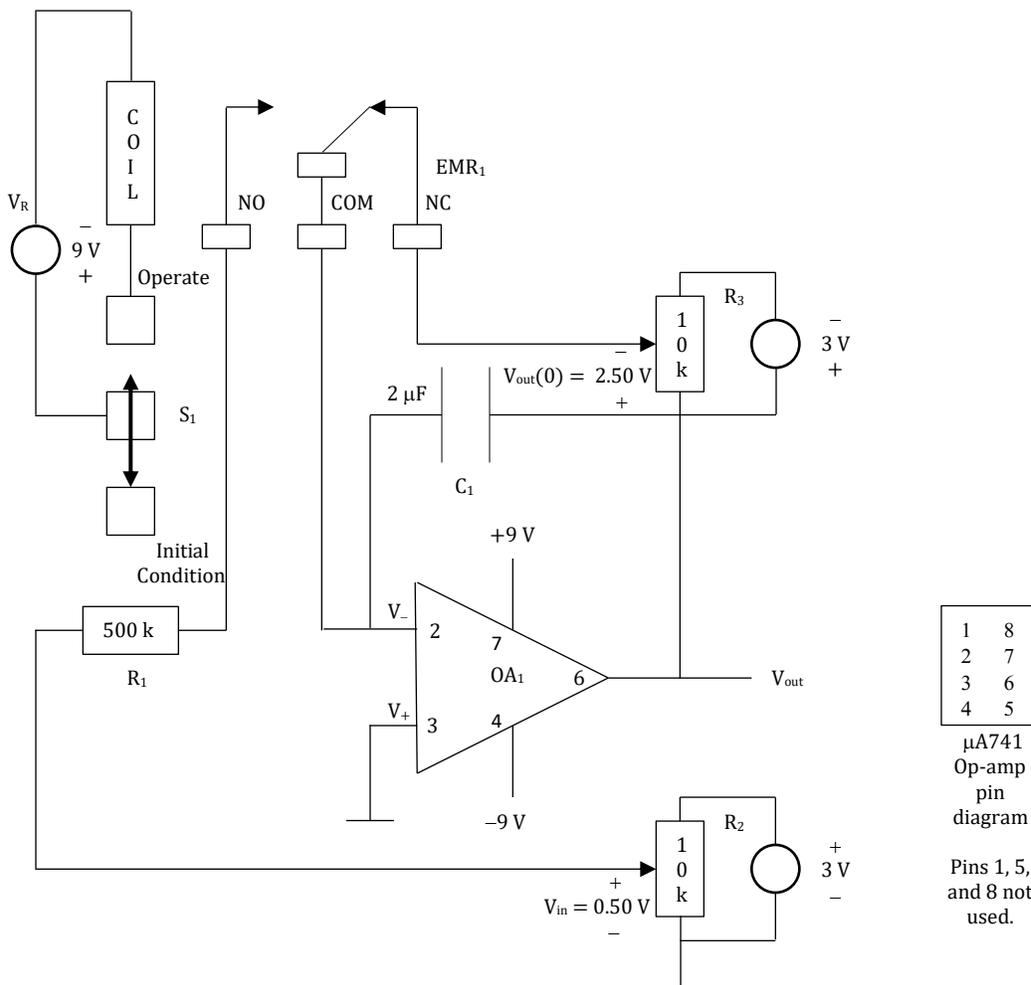


# Home-Constructed, Building Block Op-Amp Circuits for Analog Computers

## Inverting Integrator

### Introduction

Assuming the reader to be familiar with basic DC electronic theory, breadboards, ideal op-amp parameters, and a bit of calculus, the mission of this project is show him/her a circuit that performs integration! Below, is my home-constructed inverting integrator circuit. However, don't just take my word for it. Using this document as a guide, construct and test your own inverting integrator and see for yourself! Doing builds understanding! 😊 At the end of this document is a list of components and supplies used for this building block.



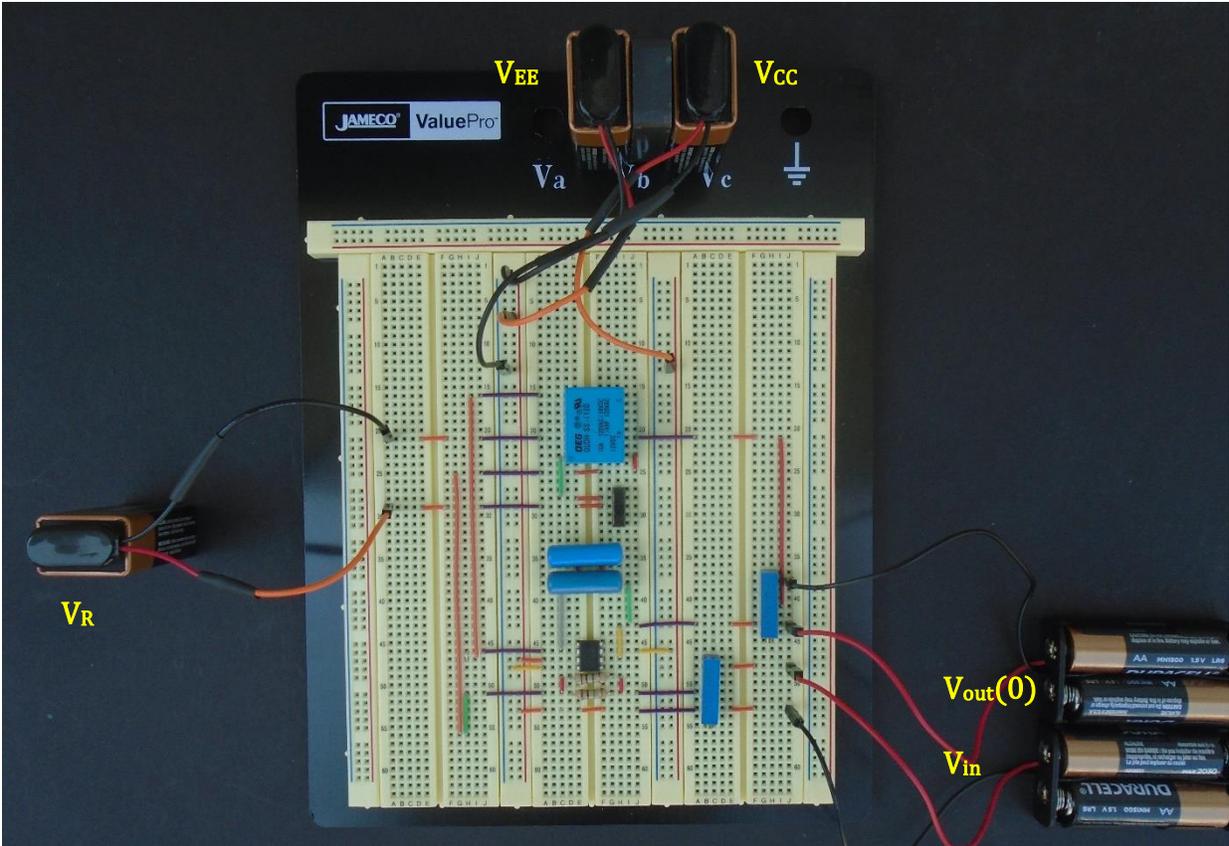


Figure 2: Photograph of inverting integrator breadboard layout

To see how this circuit integrates, I begin with a set of general current-voltage equations:

$$I_R = V_R/R,$$

where  $I_R$  is the current passing through the resistor.

Also,

$$I_C = dQ_C/dt = CdV_C/dt,$$

where  $I_C$  is the rate at which charge is deposited/removed from the capacitor. It is **NOT** charge passing through the capacitor! That would be a bad thing! 😞

Now, for a bit of op-amp circuit mathematics:

To start,

$$V_+ = V_- = 0 \text{ (virtual ground at pin 2)}$$

Determine  $I_{R1}$ :

$$I_{R1} = (V_{in} - 0)/R_1$$

$$I_{R1} = V_{in}/R_1$$

Determine  $I_{C1}$

$$I_{C1} = C_1 dV_C/dt$$

$$I_{C1} = C_1 d(0 - V_{out})/dt$$

$$I_{C1} = -C_1 dV_{out}/dt$$

Since  $R_1$  and  $C_1$  are in series (no current should flow into pin 2 of the op-amp),

$$I_{C1} = I_{R1}$$

$$-C_1 dV_{out}/dt = V_{in}/R_1$$

$$dV_{out} = -1/(R_1 C_1) V_{in} dt$$

$$\int_{V_{out}(0)}^{V_{out}} dV_{out} = -1/(R_1 C_1) \int_0^t V_{in} dt$$

Integrating and inserting limits,

$$V_{out} = -1/(R_1 C_1) \int_0^t V_{in} dt + V_{out}(0) \quad (1)$$

Tada! So, there it is ... integration! Notice the negative sign preceding the integral. Hence the term, inverting integrator!

Component nominal values:  $R_1 = 500 \text{ k} = 0.5 \times 10^6 \Omega$ ,  $C_1 = 2 \times 10^{-6} \text{ C}$ , ( $R_1 C_1 = 1 \text{ s}$ ),  $V_{out}(0) = 2.50 \text{ V}$ , and  $V_{in} = 0.50 \text{ V}$ .

After integrating and inserting component values, the nominal output voltage is

$$V_{out} = (-0.50 \text{ V/s}) t + 2.50 \text{ V} \quad (2)$$

### Data

t (s)	V <sub>out</sub> (V) Trial 1	V <sub>out</sub> (V) Trial 2	V <sub>out</sub> (V) Trial 3	V <sub>out</sub> (V) Average
00.0	+2.50	+2.50	+2.50	+2.50
05.0	+0.62	+0.62	+0.59	+0.61
10.0	-1.98	-2.00	-1.96	-1.98
15.0	-4.38	-4.43	-4.46	-4.43

Table 1: Output voltage

### Results

Using the above data, and using LinReg option on a TI-84 Plus calculator,

$$V_{\text{out}} = (-0.47 \text{ V/s}) t + 2.68 \text{ V with } r^2 = 0.996 \text{ (good fit!)} \quad (3)$$

### Conclusion

This circuit performed as expected!

---

Any questions/comments regarding this building block may be addressed to:

Michael Cimatorosi  
Physics Instructor (adjunct)  
Division of Physics, Engineering, Mathematics, and Computer Science  
Delaware State University  
Dover, DE  
Email: [mcimatorosi@desu.edu](mailto:mcimatorosi@desu.edu).

## Components

Circuit designation	Description
R <sub>1A</sub>	1 MΩ = 1000 kΩ = 1000 k
R <sub>1B</sub>	1 MΩ = 1000 kΩ = 1000 k
R <sub>1</sub> = R <sub>1A</sub>   R <sub>1B</sub>	0.500 MΩ = 500 kΩ = 500 k (measured within 1%)
R <sub>2</sub>	15-turn 10-k potentiometer
R <sub>3</sub>	15-turn 10-k potentiometer
C <sub>1A</sub>	1 μF (Polyester film)
C <sub>1B</sub>	1 μF (Polyester film)
C <sub>1</sub> = C <sub>1A</sub>   C <sub>1B</sub>	2 μF (measured within 1%)
OA <sub>1</sub>	μA741 Op Amp *(assumed ideal)- OPA140 better option
EMR <sub>1</sub>	Electromagnetic relay
S <sub>1</sub>	SPDT slide switch
V <sub>CC</sub>	+9 V (measured within 5%)
V <sub>EE</sub>	-9 V (measured within 5%)
V <sub>R</sub>	9 V relay voltage (measured within 5%)
V <sub>in</sub>	+0.50 V (adjusted)
V <sub>out(0)</sub>	+2.50 V (adjusted)

## Miscellaneous Supplies

Item	Quantity
Fixed jumper wire kit	1
3-section breadboard	1
Digital multimeter	1
Timepiece	1
9-Volt batteries	2
1.5-Volt batteries	4
3-Volt battery case with leads	2
30-Volt (max) DC supply	1
Ti-84 Plus calculator	1
Magnet	1

August 26, 2021